



Figure 7.48 The principle of the global error feedforward amplifier that was prototyped.  $A_1$  and  $A_3$  are both simple power amplifiers. The error amplifier with a gain of 100 V/V was built using AD797 operational amplifiers.